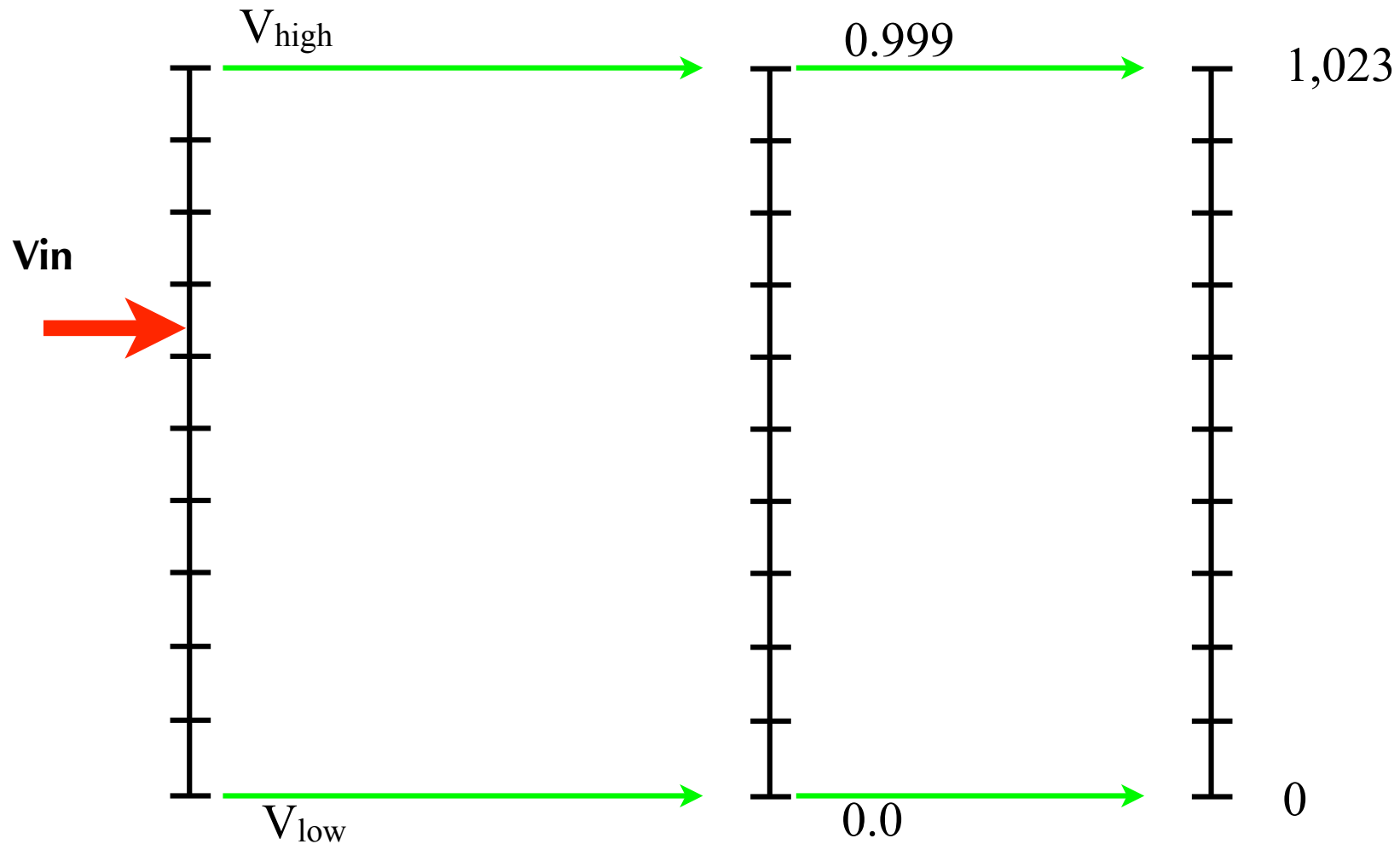


Analog to Digital Conversion

Gary J. Minden
October 1, 2013




Mapping Input Voltage to Digital Value




Analog to Digital Conversion

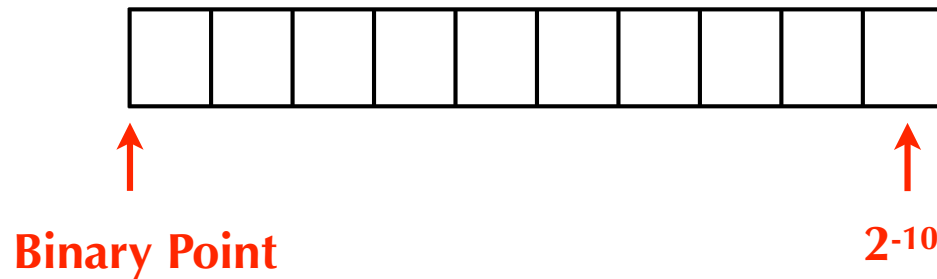
- Analog -- A voltage between V_{low} and V_{high}
- Digital -- A fraction between 0.0 and 1.0 with K bits
 - In the case of the LM3S1968, $K = 10$ and there are 1,024 steps.
 - Fraction: Values between 0.0 and 0.999023



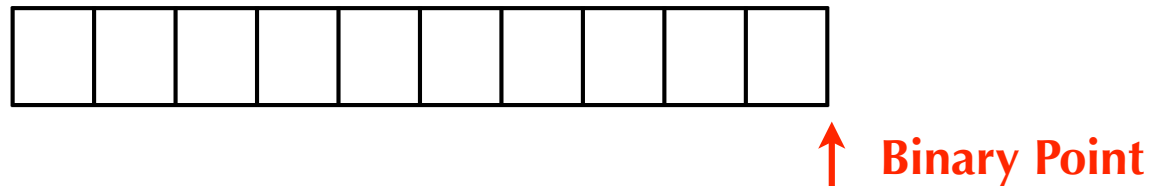- Integer: Values between 0 and 1,023 with scale factor of 2^{-10}




Challenge #1 -- Compare Voltage

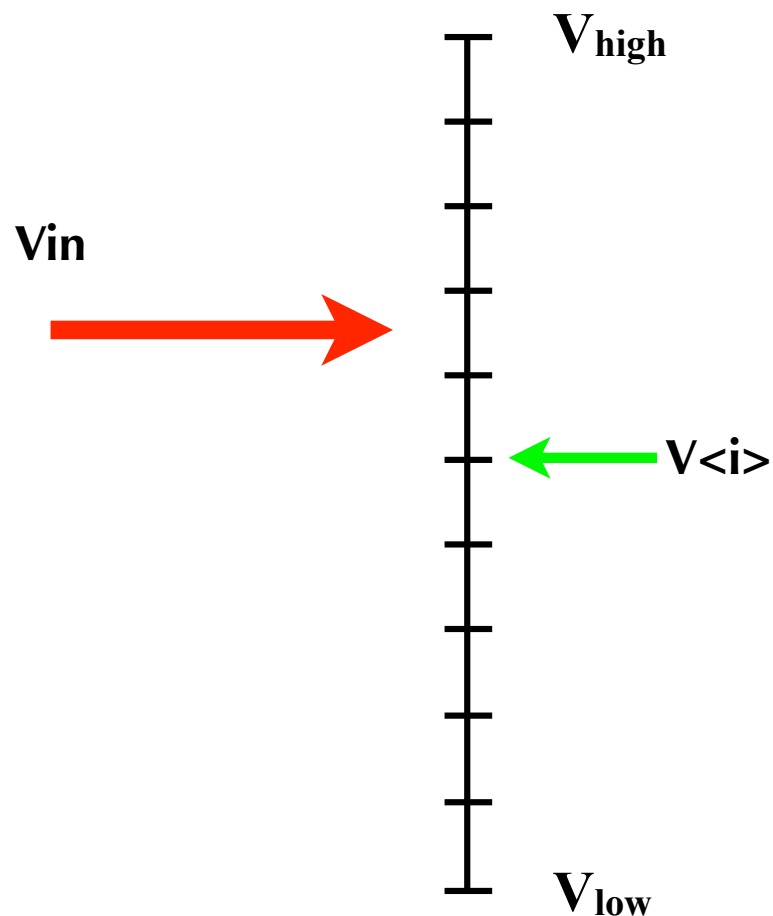


- V_{in} is input Voltage
- Range is V_{low} to V_{high}
- $V_{\langle i \rangle}$ is “test” Voltage
- How to compare V_{in} to $V_{\langle i \rangle}$?
- That is, is $V_{\text{in}} < V_{\langle i \rangle}$ or not?

Comparator

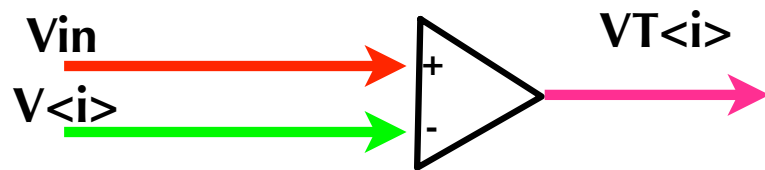


- If $V_{in} > V_{<i>$, then $VT_{<i>$ is True (1)
- A logic signal

Array of Comparators

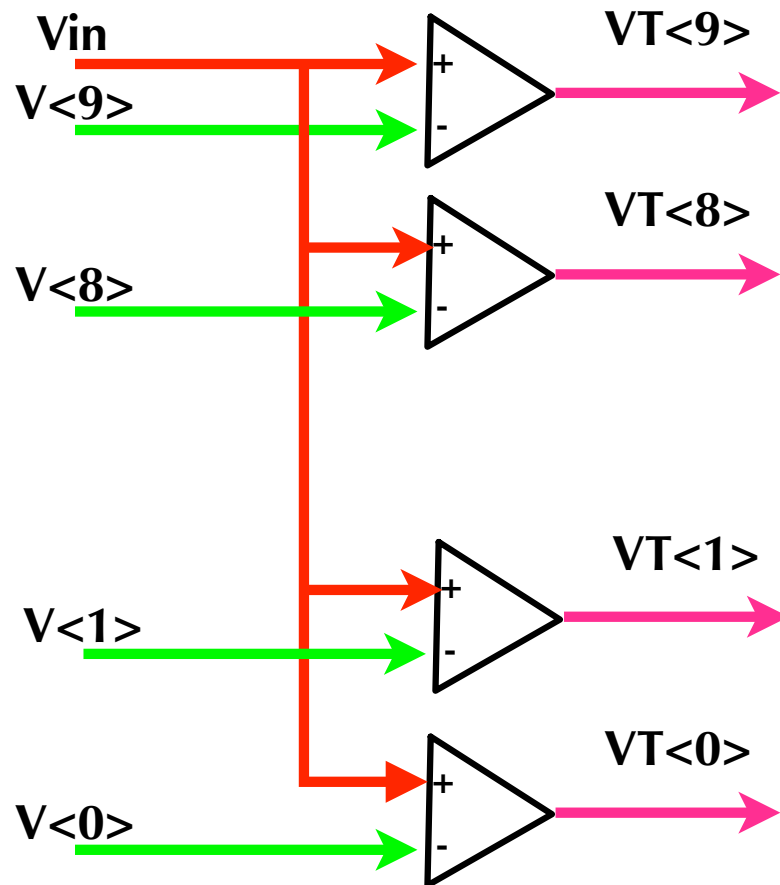

- Set up array of comparators
- Each comparator tests V_{in}
- Each has a different $V<i>$
- Each comparator generates a logic value, 0 or 1

Results

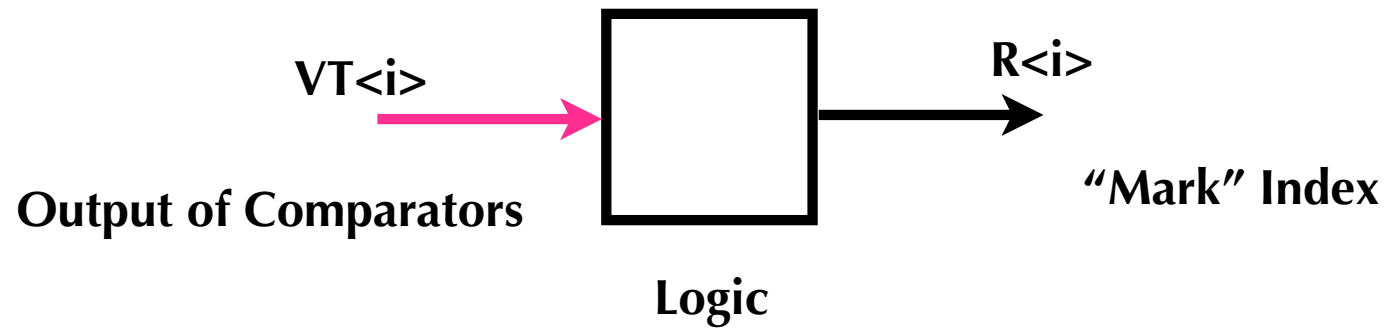


V<9>	V<8>	V<7>	V<6>	V<5>	V<4>	V<3>	V<2>	V<1>	V<0>	R<3>	R<2>	R<1>	R<0>
0	0	0	0	1	1	1	1	1	1	0	1	0	1
0	0	0	0	0	0	0	1	1	1	0	0	1	0
0	1	1	1	1	1	1	1	1	1	1	0	0	0
0	0	0	0	0	0	0	0	0	0	0	0	0	0

Problems and Approach


- This does not scale for a large number of “steps”
 - E.g. 1,024 or 4,096
- Successively generate $V_{<i>}$, a test Voltage, over several trials
 - What sequence of $V_{<i>}$ to use
 - How do you generate $V_{<i>}$?

Successive Approximation Approach #1

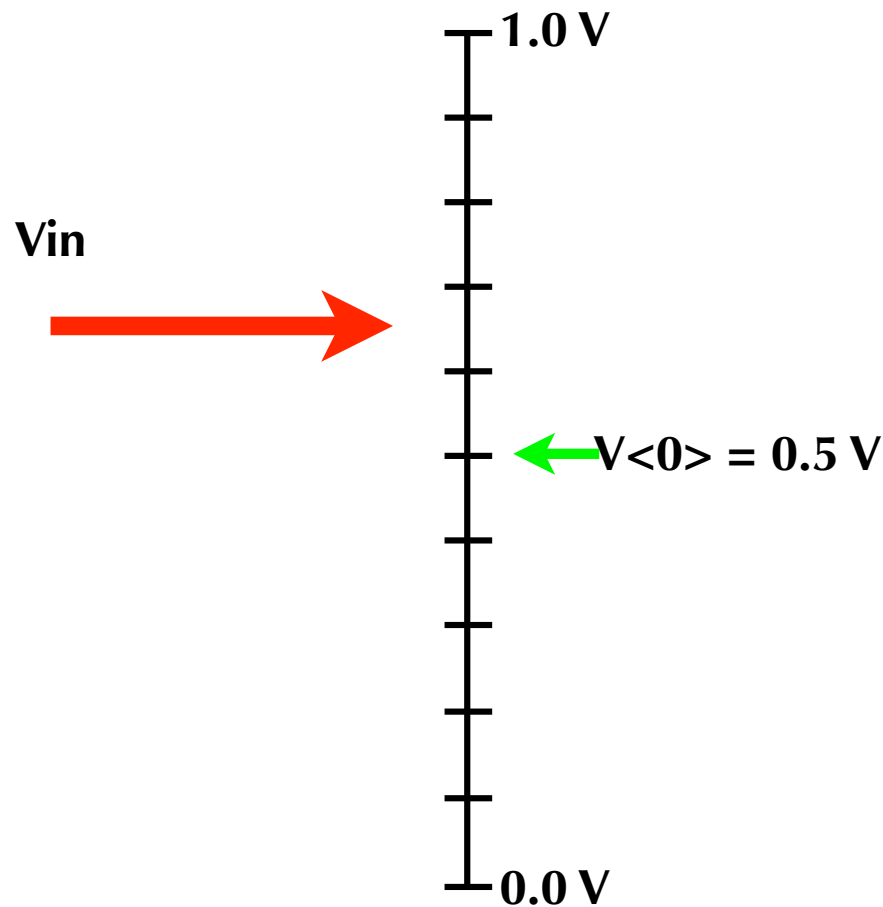


- V_{in} is input Voltage
- Range is 0.0 - 1.0 V
- Assume 1,024 steps
- $V_{<0>}$ is first test Voltage
- Start in the middle
- If $V_{in} < V_{<0>}$, decrease test voltage
- If $V_{in} \geq V_{<0>}$, increase test voltage
- **$V_{in} > V_{<0>}$, increase**

Successive Approximation Approach #2

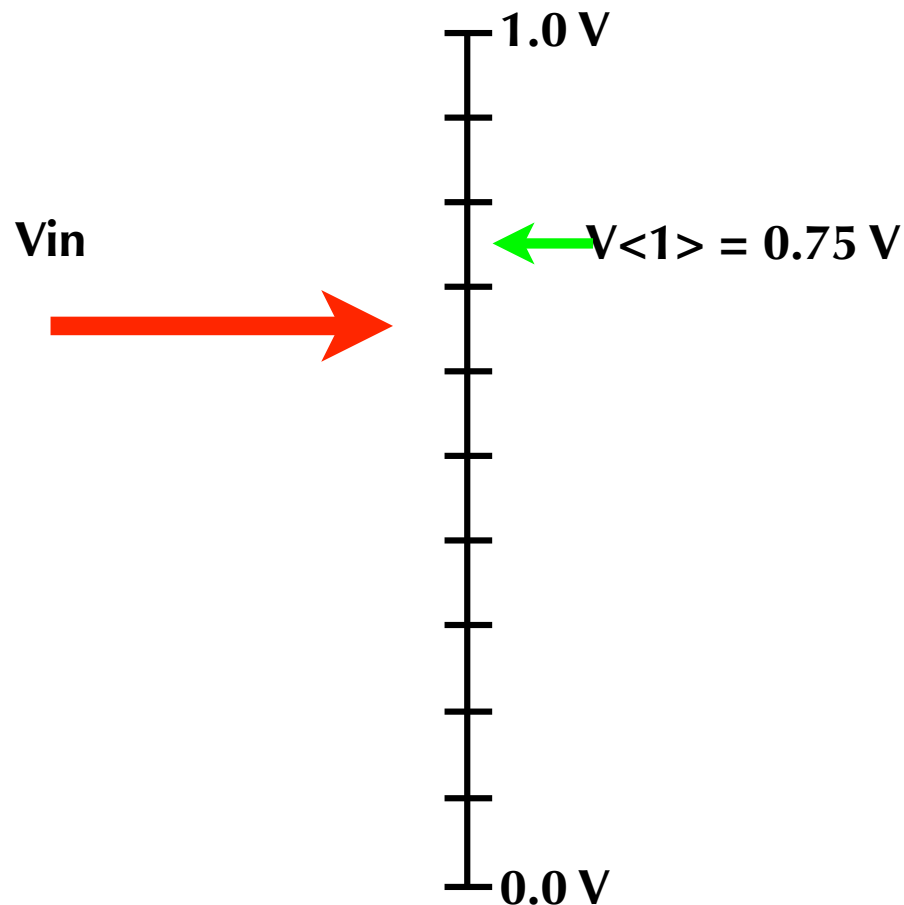


- V_{in} is input Voltage
- Range is 0.0 - 1.0 V
- Assume 1,024 steps
- $V_{<1>}$ is test voltage
- If $V_{in} < V_{<1>}$, decrease test voltage
- If $V_{in} \geq V_{<1>}$, increase test voltage
- **$V_{in} < V_{<1>}$, decrease test voltage**

Successive Approximation Approach #3

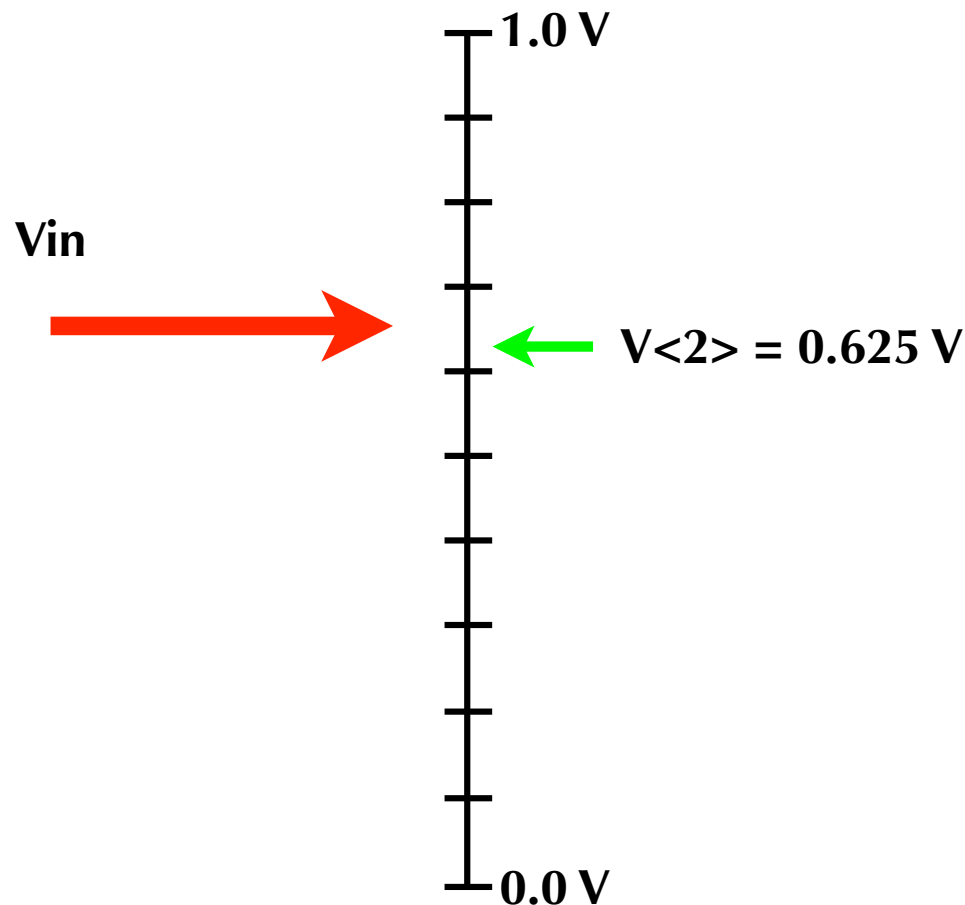

- V_{in} is input Voltage
- Range is 0.0 - 1.0 V
- Assume 1,024 steps
- $V_{<2>}$ is test voltage
- Start in the middle
- If $V_{in} < V_{<2>}$, decrease $V_{<i>}$
- If $V_{in} \geq V_{<2>}$, increase $V_{<i>}$
- **$V_{in} \geq V_{<2>}$, increase**


Successive Approximation Approach #10

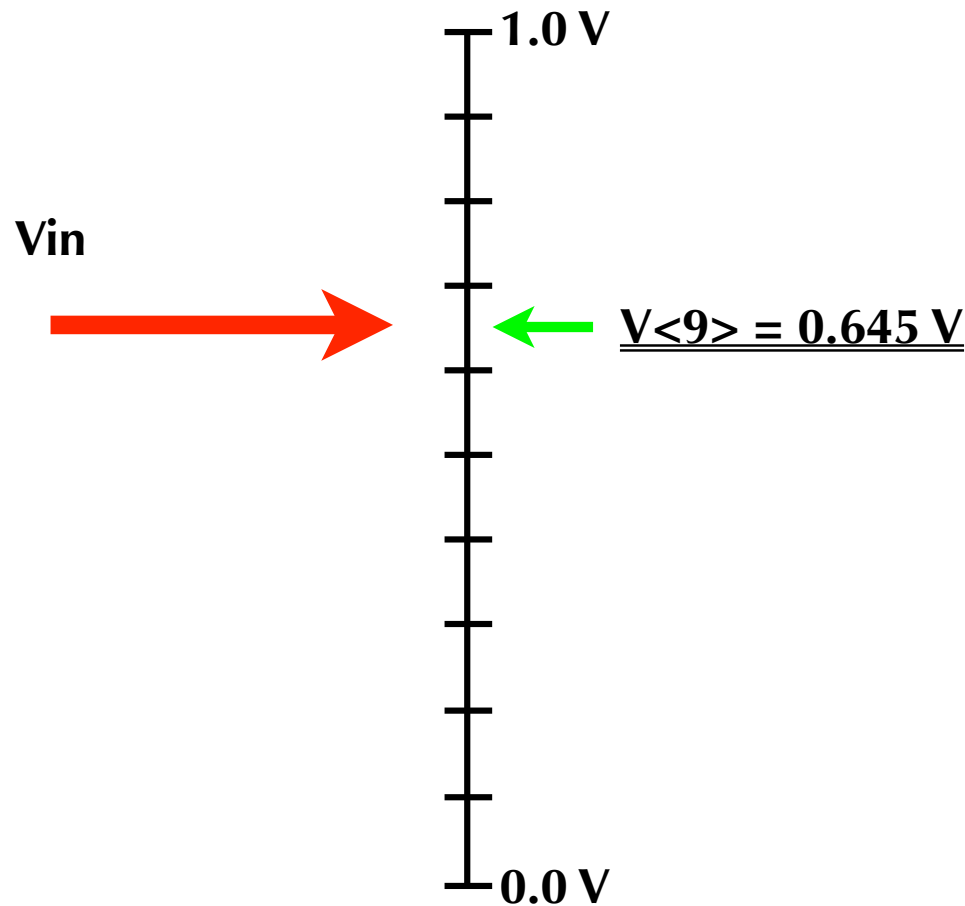

- V_{in} is input Voltage
- Range is 0.0 - 1.0 V
- Assume 1,024 steps
- $V_{<9>}$ is test Voltage
- If $V_{in} < V_{<9>}$, decrease test voltage
- If $V_{in} \geq V_{<9>}$, increase test voltage
- **Done**

Successive Approach with DAC

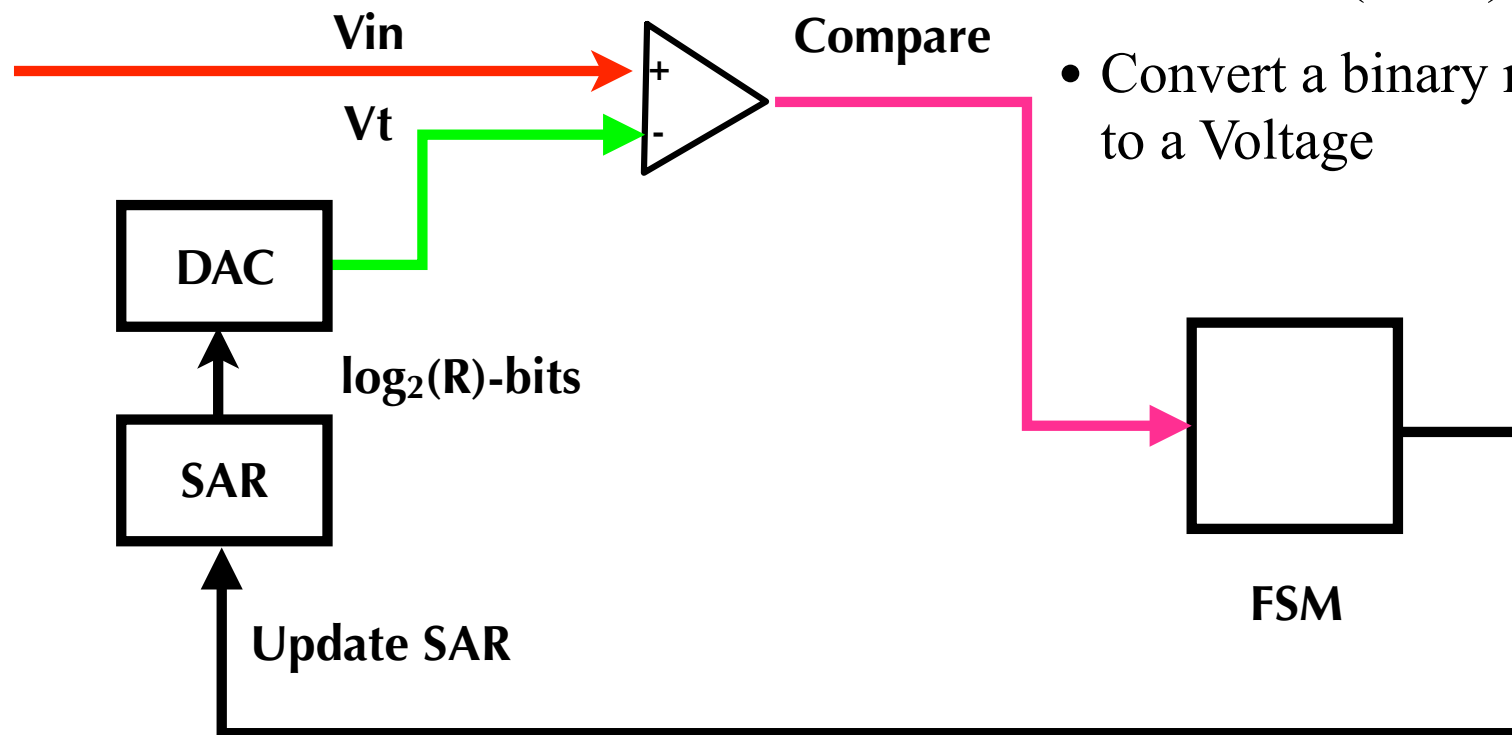- Generate $V_{(i)}$ with a Digital to Analog Converter (DAC)
- Convert a binary number to a Voltage



Example with $V_{in} = 0.644$ V

i	s<9>	s<8>	s<7>	s<6>	s<5>	s<4>	s<3>	s<2>	s<1>	s<0>	V<i>	Comp
0	1	0	0	0	0	0	0	0	0	0	0.5	1
1	1	1	0	0	0	0	0	0	0	0	0.75	0
2	1	0	1	0	0	0	0	0	0	0	0.625	1
3	1	0	1	1	0	0	0	0	0	0	0.688	0
4	1	0	1	0	1	0	0	0	0	0	0.656	0
5	1	0	1	0	0	1	0	0	0	0	0.641	1
6	1	0	1	0	0	1	1	0	0	0	0.648	0
7	1	0	1	0	0	1	0	1	0	0	0.645	0
8	1	0	1	0	0	1	0	0	1	0	0.643	1
9	1	0	1	0	0	1	0	0	1	1	0.644	1
D	1	0	1	0	0	1	0	0	1	1	0.644	

Compare == 1 if $V_{in} \geq V_{<i>}$

Example with $V_{in} = 0.644$ V

i	s<9>	s<8>	s<7>	s<6>	s<5>	s<4>	s<3>	s<2>	s<1>	s<0>	V<i>	Comp
0	1	0	0	0	0	0	0	0	0	0	0.5	1
1	1	1	0	0	0	0	0	0	0	0	0.75	0
2	1	0	1	0	0	0	0	0	0	0	0.625	1
3	1	0	1	1	0	0	0	0	0	0	0.688	0
4	1	0	1	0	1	0	0	0	0	0	0.656	0
5	1	0	1	0	0	1	0	0	0	0	0.641	1
6	1	0	1	0	0	1	1	0	0	0	0.648	0
7	1	0	1	0	0	1	0	1	0	0	0.645	0
8	1	0	1	0	0	1	0	0	1	0	0.643	1
9	1	0	1	0	0	1	0	0	1	1	0.644	1
D	1	0	1	0	0	1	0	0	1	1	0.644	

Compare == 1 if $V_{in} \geq V_{<i>}$

Example with $V_{in} = 0.644$ V

i	s<9>	s<8>	s<7>	s<6>	s<5>	s<4>	s<3>	s<2>	s<1>	s<0>	V<i>	Comp
0	1	0	0	0	0	0	0	0	0	0	0.5	1
1	1	1	0	0	0	0	0	0	0	0	0.75	0
2	1	0	1	0	0	0	0	0	0	0	0.625	1
3	1	0	1	1	0	0	0	0	0	0	0.688	0
4	1	0	1	0	1	0	0	0	0	0	0.656	0
5	1	0	1	0	0	1	0	0	0	0	0.641	1
6	1	0	1	0	0	1	1	0	0	0	0.648	0
7	1	0	1	0	0	1	0	1	0	0	0.645	0
8	1	0	1	0	0	1	0	0	1	0	0.643	1
9	1	0	1	0	0	1	0	0	1	1	0.644	1
D	1	0	1	0	0	1	0	0	1	1	0.644	

Compare == 1 if $V_{in} \geq V_{<i>}$

Example with $V_{in} = 0.644$ V

i	s<9>	s<8>	s<7>	s<6>	s<5>	s<4>	s<3>	s<2>	s<1>	s<0>	V<i>	Comp
0	1	0	0	0	0	0	0	0	0	0	0.5	1
1	1	1	0	0	0	0	0	0	0	0	0.75	0
2	1	0	1	0	0	0	0	0	0	0	0.625	1
3	1	0	1	1	0	0	0	0	0	0	0.688	0
4	1	0	1	0	1	0	0	0	0	0	0.656	0
5	1	0	1	0	0	1	0	0	0	0	0.641	1
6	1	0	1	0	0	1	1	0	0	0	0.648	0
7	1	0	1	0	0	1	0	1	0	0	0.645	0
8	1	0	1	0	0	1	0	0	1	0	0.643	1
9	1	0	1	0	0	1	0	0	1	1	0.644	1
D	1	0	1	0	0	1	0	0	1	1	0.644	

Compare == 1 if $V_{in} \geq V_{<i>}$

Result Value Format

Scale Factor




2^{-1}	2^{-2}	2^{-3}	2^{-4}	2^{-5}	2^{-6}	2^{-7}	2^{-8}	2^{-9}	2^{-10}
$1/2$	$1/4$	$1/8$	$1/16$	$1/32$	$1/64$	$1/128$	$1/256$	$1/512$	$1/1024$
1	0	1	0	0	1	0	0	1	1



Binary Point


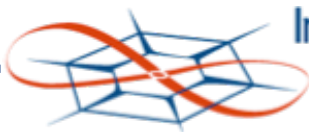
$$R = 1/2 + 1/8 + 1/64 + 1/512 + 1/1024 = 0.644$$



Information and
Telecommunication
Technology Center


KU THE UNIVERSITY OF
KANSAS

ADC Architecture

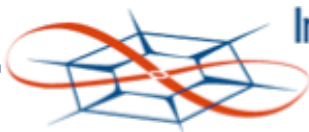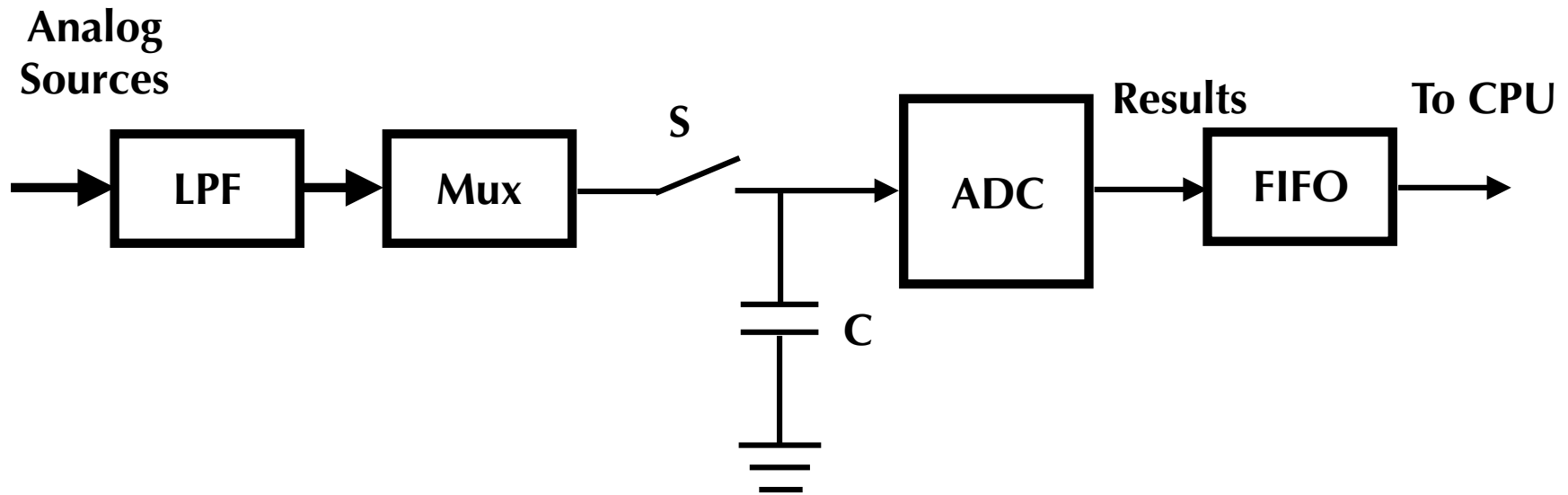

Successive Approach with DAC


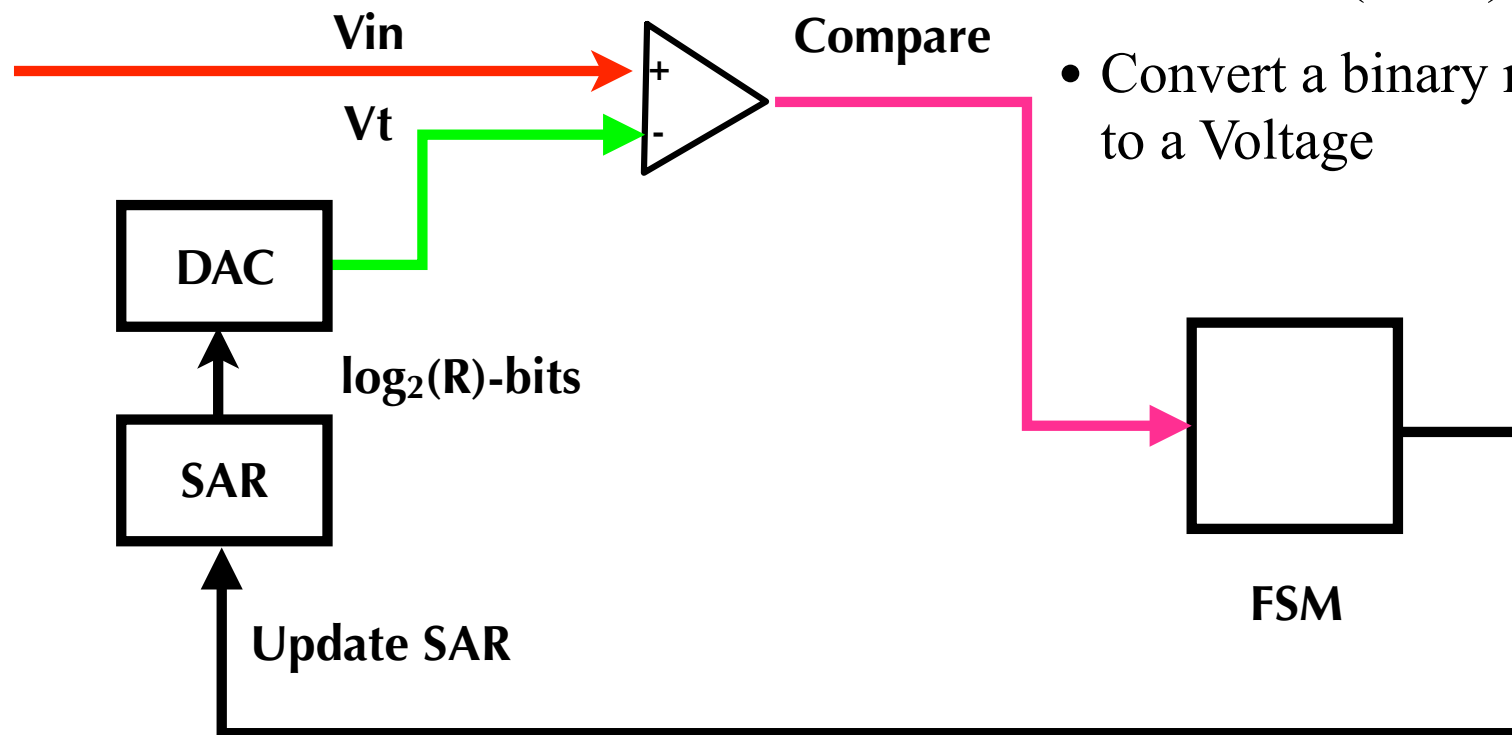
- Generate $V_{(i)}$ with a Digital to Analog Converter (DAC)
- Convert a binary number to a Voltage



Measured Voltage

$$V_{\text{Measured}} = R * V_{\text{Ref}}$$

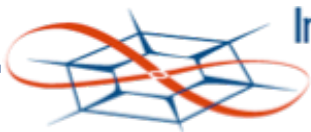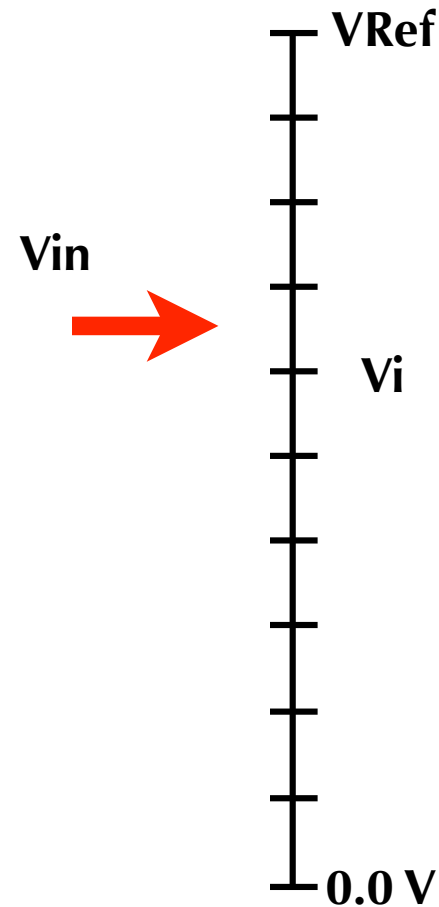
Internal $V_{\text{Ref}} = 3.0 \text{ V}$



LM3S1968 ADC Features

- Eight analog input channels
- Single-ended and differential-input configurations
- On-chip internal temperature sensor
- Sample rate of one million samples/second
- Four programmable sample conversion sequences from one to eight entries long, with corresponding conversion result FIFOs
- Flexible trigger control
 - Controller (software), Timers, Analog Comparators, PWM, GPIO
- Hardware averaging of up to 64 samples for improved accuracy
- Converter uses an internal 3-V reference
- Power and ground for the analog circuitry is separate from the digital power and ground

Stellaris ADC Architecture

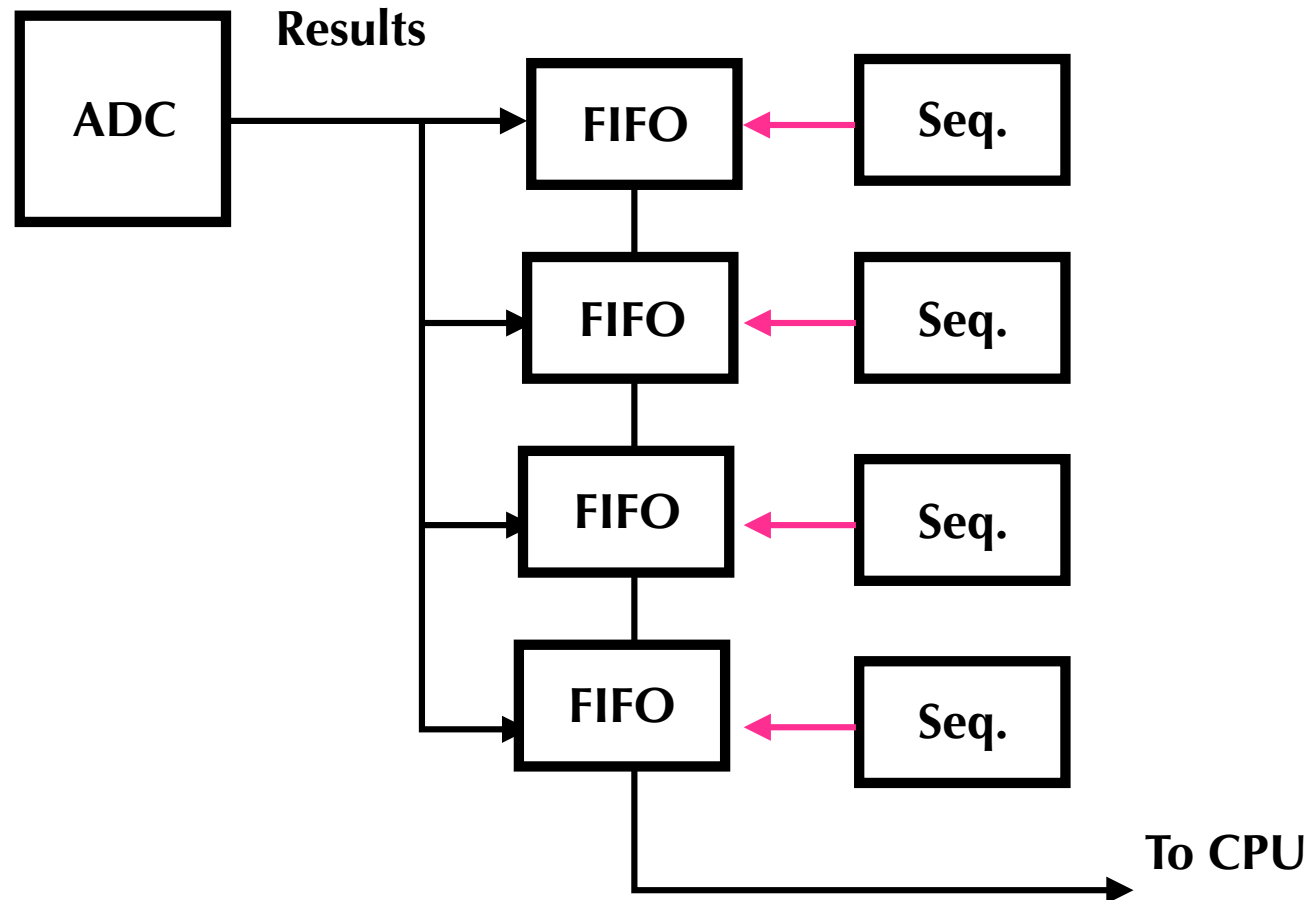


ADC Control

- Enable
- Interrupt generation
- DMA operation
- Sequence prioritization
 - Each sequencer has a priority, 0-3, 0 is highest
- Trigger configuration
 - Processor (default), analog comparators, an external signal on GPIO PB4 , a GP Timer, a PWM generator, and continuous sampling.
- Comparator configuration
- External voltage reference
- Sample phase control

LM3S1968 ADC Block Diagram

Figure 11-1. ADC Module Block Diagram

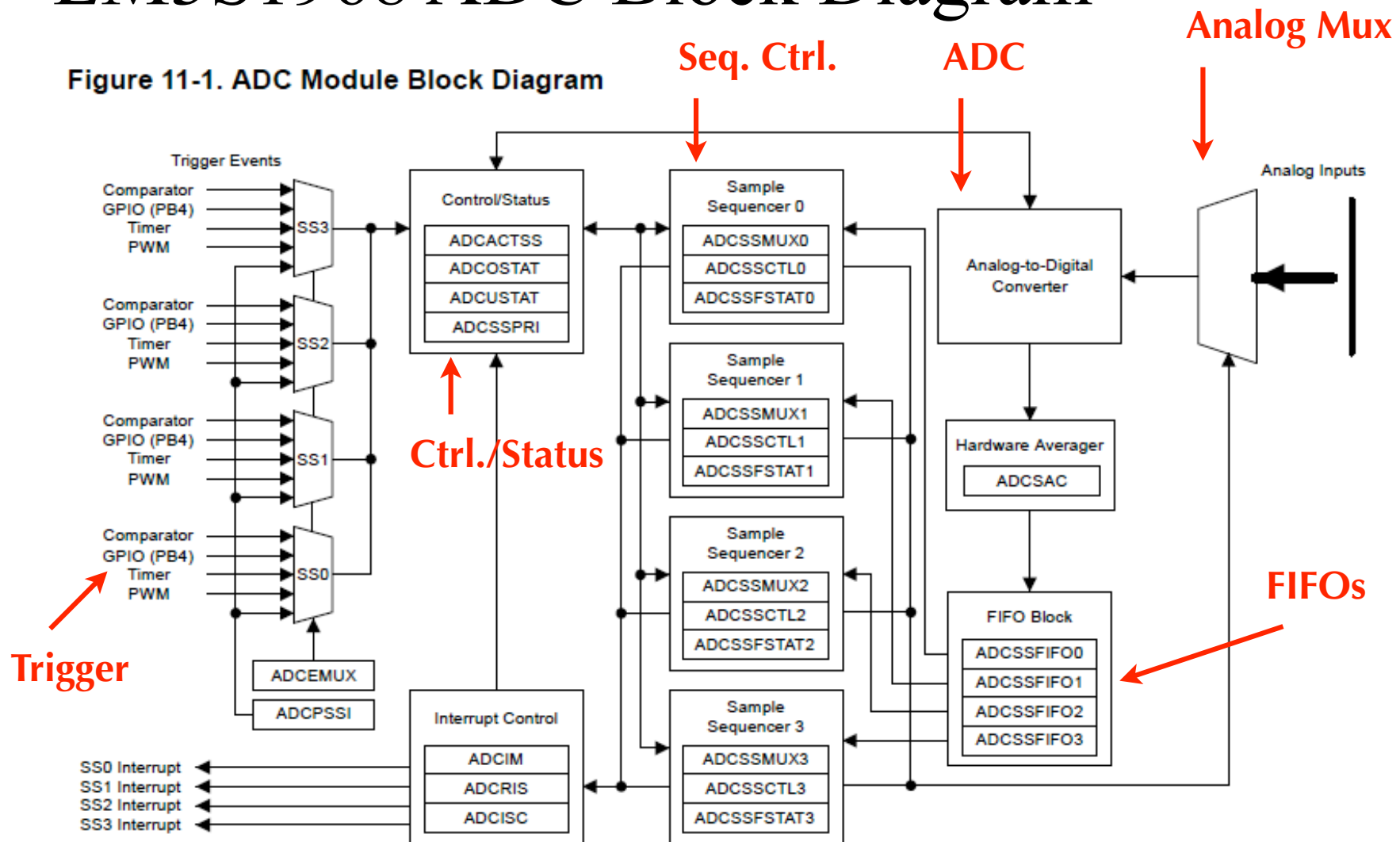

ADC Sequencer Characteristics

Table 11-3. Samples and FIFO Depth of Sequencers

Sequencer	Number of Samples	Depth of FIFO
SS3	1	1
SS2	4	4
SS1	4	4
SS0	8	8

Most of the ADC control logic runs at the ADC clock rate of 14-18 MHz. The internal ADC divider is configured automatically by hardware when the system XTAL is selected. The automatic clock divider configuration targets 16.667 MHz operation for all Stellaris devices.

Differential Inputs

Table 11-4. Differential Sampling Pairs

Differential Pair	Analog Inputs
0	0 and 1
1	2 and 3
2	4 and 5
3	6 and 7

The voltage sampled in differential mode is the difference between the odd and even channels:

ΔV (differential voltage) = V_{IN_EVEN} (even channels) – V_{IN_ODD} (odd channels), therefore:



- If $\Delta V = 0$, then the conversion result = 0x1FF
- If $\Delta V > 0$, then the conversion result > 0x1FF (range is 0x1FF–0x3FF)
- If $\Delta V < 0$, then the conversion result < 0x1FF (range is 0–0x1FF)

The differential pairs assign polarities to the analog inputs: the even-numbered input is always positive, and the odd-numbered input is always negative. In order for a valid conversion result to appear, the negative input must be in the range of ± 1.5 V of the positive input. If an analog input is greater than 3 V or less than 0 V (the valid range for analog inputs), the input voltage is clipped, meaning it appears as either 3 V or 0 V, respectively, to the ADC.

Differential Inputs

$$\text{deltaV} = \text{ADCeven} - \text{ADCodd}$$

Used for common voltage rejection

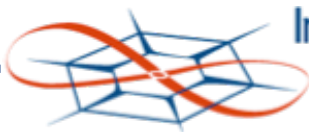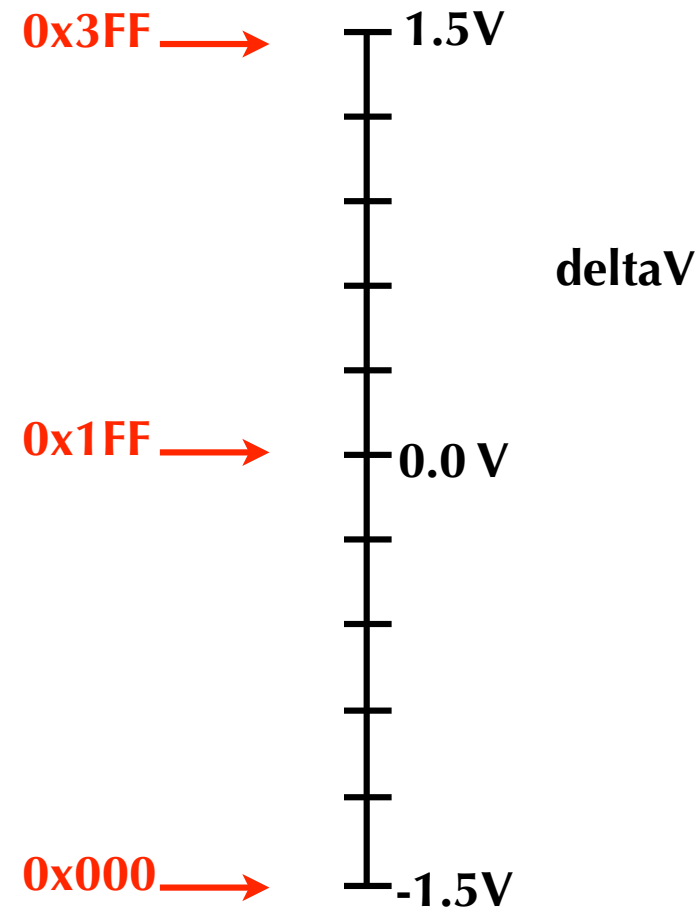

Information and
Telecommunication
Technology Center

KU THE UNIVERSITY OF
KANSAS

ADC Initialization

Enable ADC0

```
unsigned long ulValue;
```

```
SysCtlPeripheralEnable( SYSCTL_PERIPH_ADC0 );
```

Config. ADC0/Seq0 Prog. Trig.

```
//
```

```
// Enable the first sample sequencer to capture the value of channel 0 when  
// the processor trigger occurs.
```

```
//
```

```
ADCSequenceConfigure(ADC0_BASE, 0, ADC_TRIGGER_PROCESSOR, 0);
```

```
ADCSequenceStepConfigure(ADC0_BASE, 0, 0,  
                          ADC_CTL_IE | ADC_CTL_END | ADC_CTL_CH0);
```

```
ADCSequenceEnable(ADC0_BASE, 0);
```

```
void ADCSequenceConfigure(unsigned long ulBase,  
                          unsigned long ulSequenceNum,  
                          unsigned long ulTrigger,  
                          unsigned long ulPriority)
```

```
void ADCSequenceStepConfigure(unsigned long ulBase,  
                              unsigned long ulSequenceNum,  
                              unsigned long ulStep,  
                              unsigned long ulConfig)
```

ADC Step Configuration

```
unsigned long ulValue;
```

Config. ADC0/Seq0

```
SysCtlPeripheralEnable( SYSCTL_PERIPH_ADC0 );
```

Step Index

```
//
```

```
// Enable the first sample sequencer to capture the value of channel 0 when  
// the processor trigger occurs.
```

```
//
```

```
ADCSequenceConfigure(ADC0_BASE, 0, ADC_TRIGGER_PROCESSOR, 0);
```

```
ADCSequenceStepConfigure(ADC0_BASE, 0, 0,  
                        ADC_CTL_IE | ADC_CTL_END | ADC_CTL_CH0);
```

```
ADCSequenceEnable(ADC0_BASE, 0);
```

Int. Enable

ADC0/Ch0

Last Step

```
void ADCSequenceConfigure(unsigned long ulBase,  
                        unsigned long ulSequenceNum,  
                        unsigned long ulTrigger,  
                        unsigned long ulPriority)
```

```
void ADCSequenceStepConfigure(unsigned long ulBase,  
                        unsigned long ulSequenceNum,  
                        unsigned long ulStep,  
                        unsigned long ulConfig)
```

ADC Trigger, Wait, Read Result

```
//  
// Trigger the sample sequence.  
//  
ADCProcessorTrigger(ADC0_BASE, 0);  
  
//  
// Wait until the sample sequence has completed.  
//  
while(!ADCIntStatus(ADC0_BASE, 0, false))  
{  
}  
  
//  
// Read the value from the ADC.  
//  
ADCSequenceDataGet(ADC0_BASE, 0, &ulValue);
```

Start →



Wait →

Read Date →

Sensor Value Mapping

- Sensor is electronic device
 - Thermistor, Photo-Transistor, Microphone, ...
- Each sensor has a physical measurement range
 - E.g. -40°C to 120°C
- Each sensor maps measurement range a voltage range based on sensor and electronic circuit
 - E.g. Map -40°C to 120°C to 0.0 V to 2.5 V
- Micro-controller measures voltage
 - E.g. Voltage between 0.0 V and 3.0 V on LM3S1968
- Program has to interpret voltage measurement



Sensor to Voltage Mapping

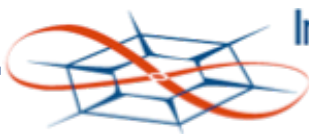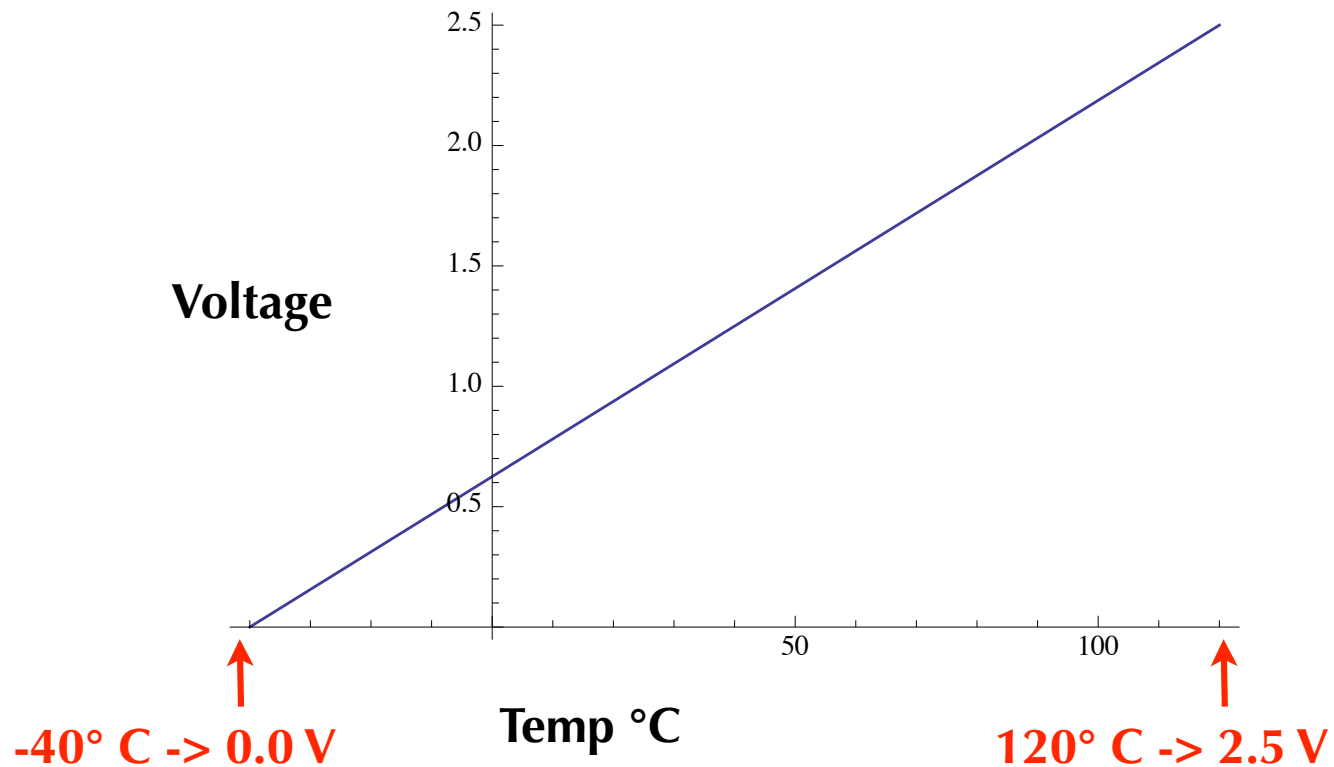

Information and
Telecommunication
Technology Center

KU THE UNIVERSITY OF
KANSAS


ADC Voltage to Value Mapping

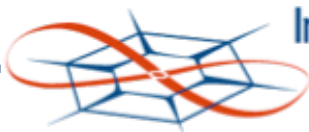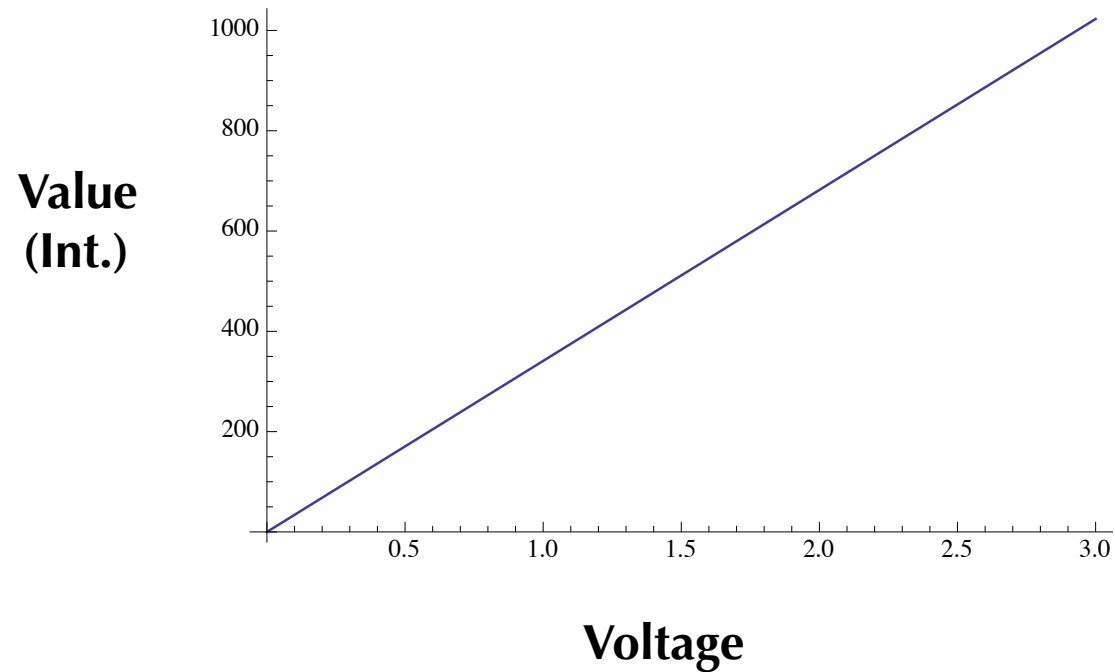



Information and
Telecommunication
Technology Center

KU THE UNIVERSITY OF
KANSAS

Sensor to Voltage Mapping

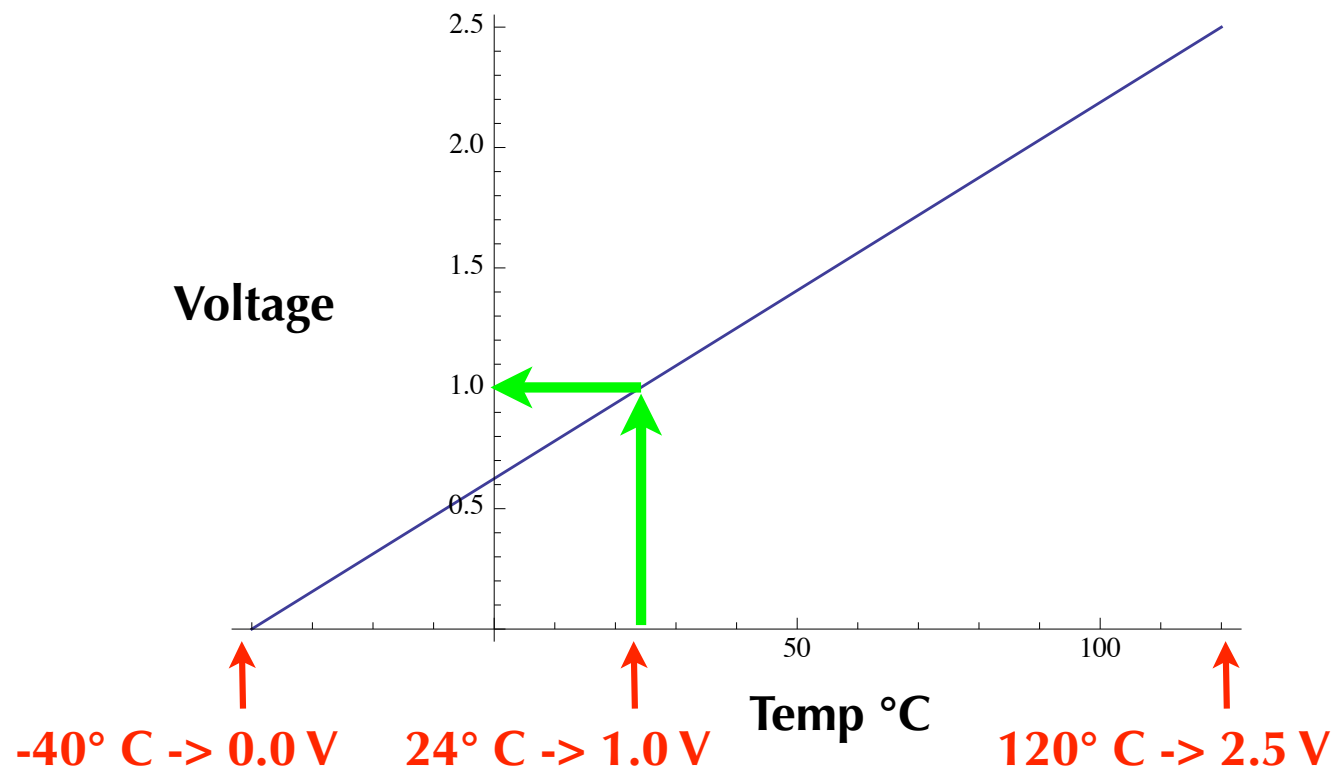

ADC Voltage to Value Mapping

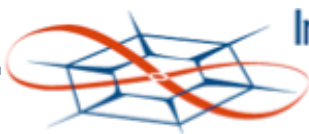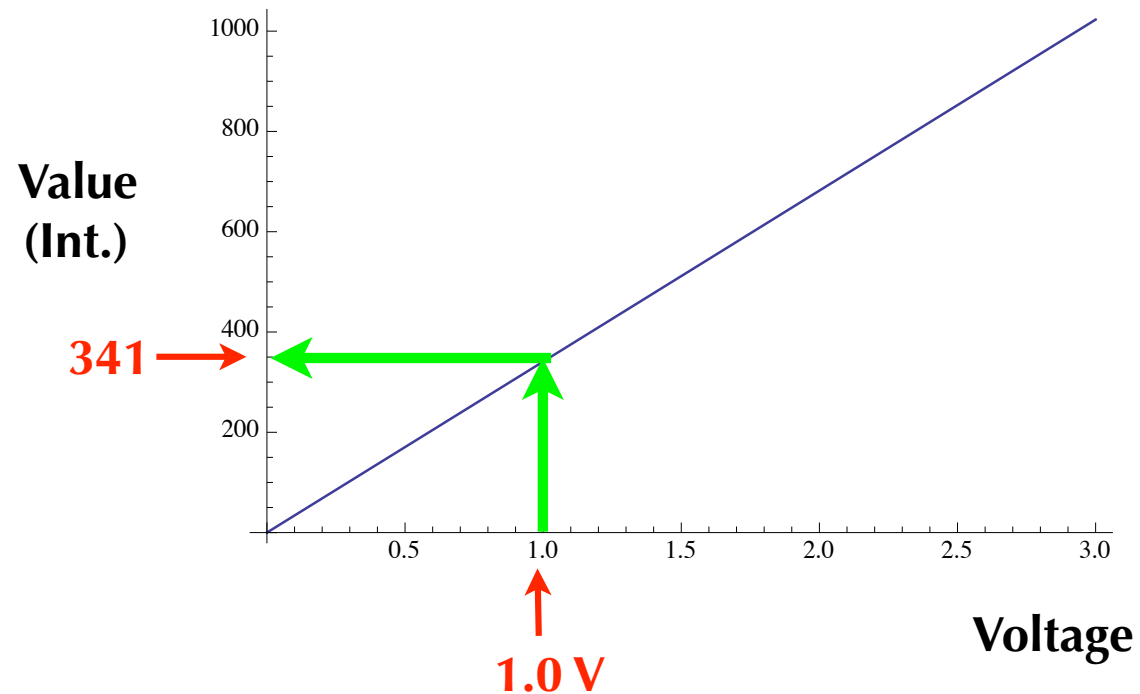


Information and
Telecommunication
Technology Center

KU THE UNIVERSITY OF
KANSAS

LM3S1968 Temperature Sensor



Figure 11-5. Internal Temperature Sensor Characteristic

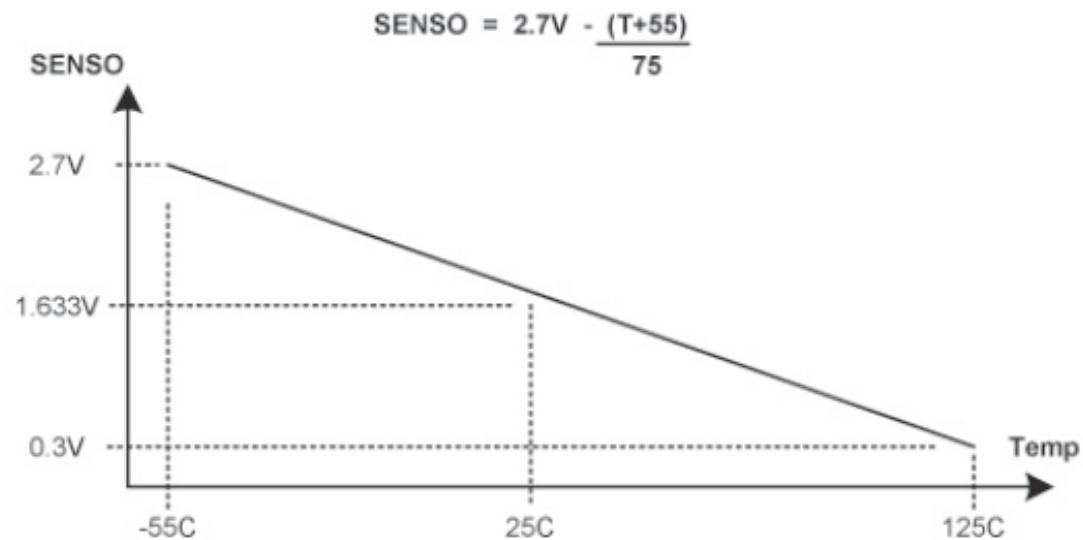



LM3S1968 Datasheet, pg. 400

LM3S1968 Temperature Sensor

Figure 11-5. Internal Temperature Sensor Characteristic

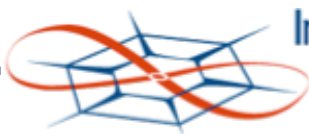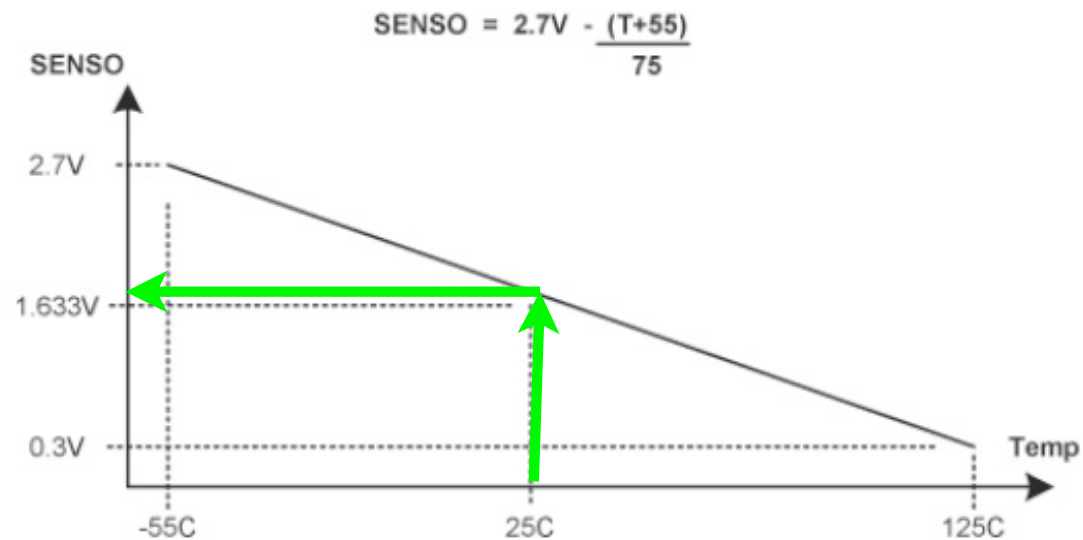


ADC Voltage to Value Mapping

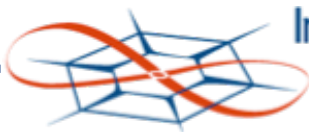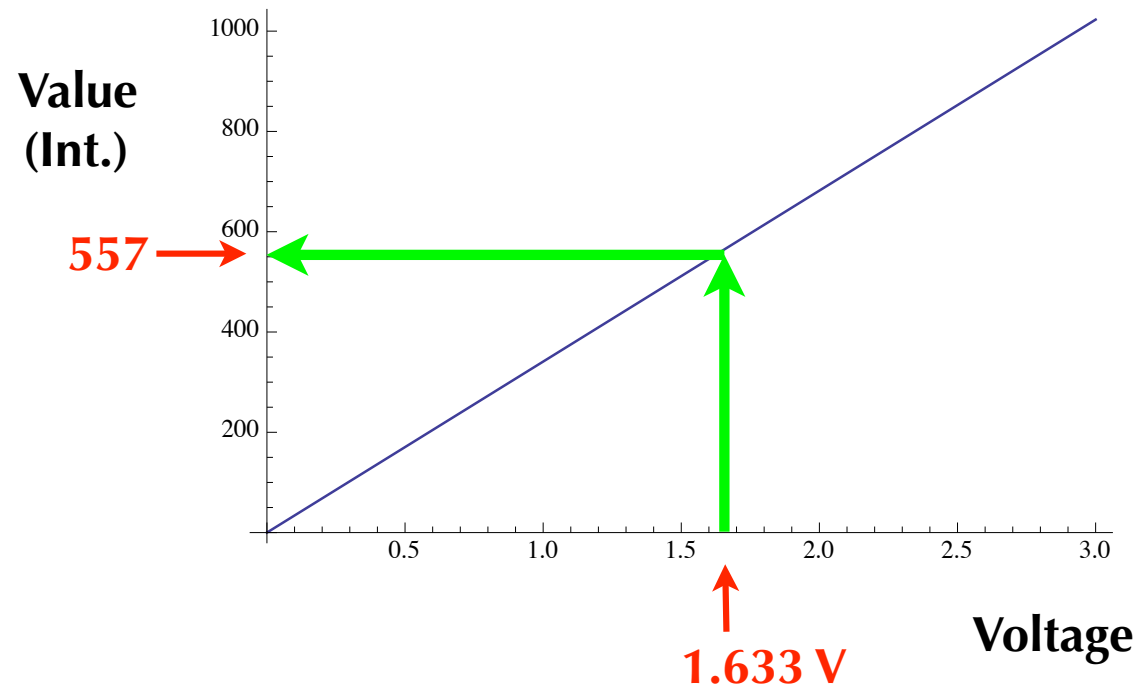

Information and
Telecommunication
Technology Center

KU THE UNIVERSITY OF
KANSAS


ADC Voltage to Value Mapping

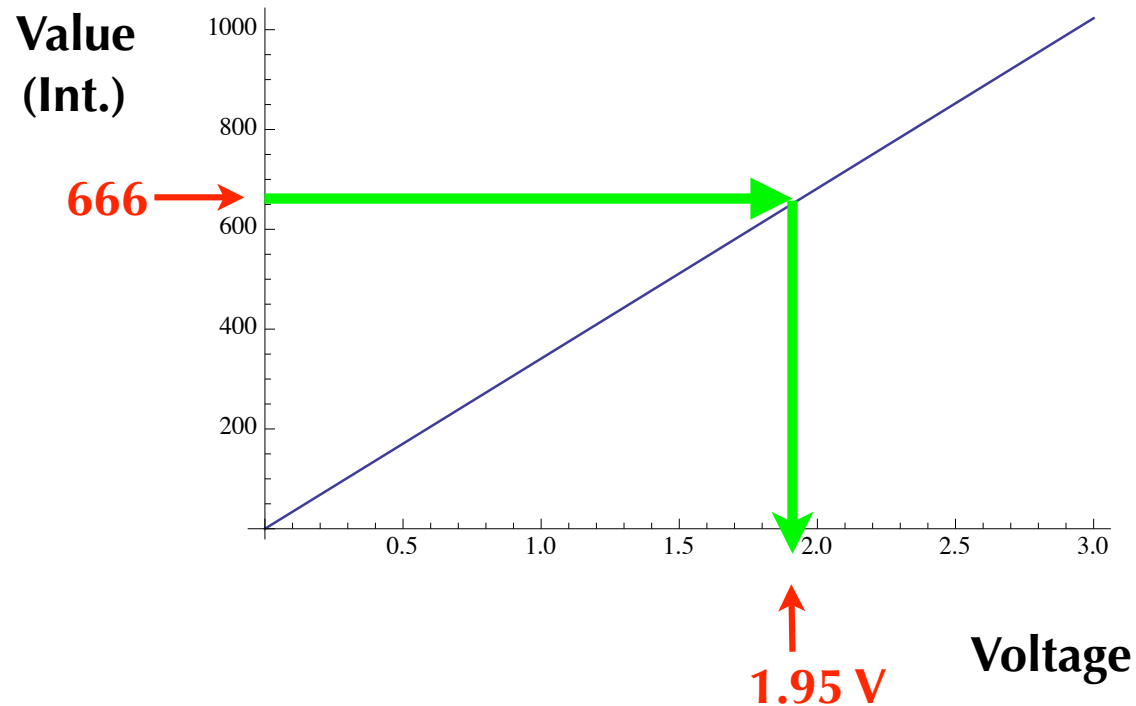

$$666/1024 * 3.0 \text{ V} = 0.6504 * 3.0 = 1.95 \text{ V} = V_{\text{Sensor}}$$

LM3S1968 Temperature Sensor



Figure 11-5. Internal Temperature Sensor Characteristic

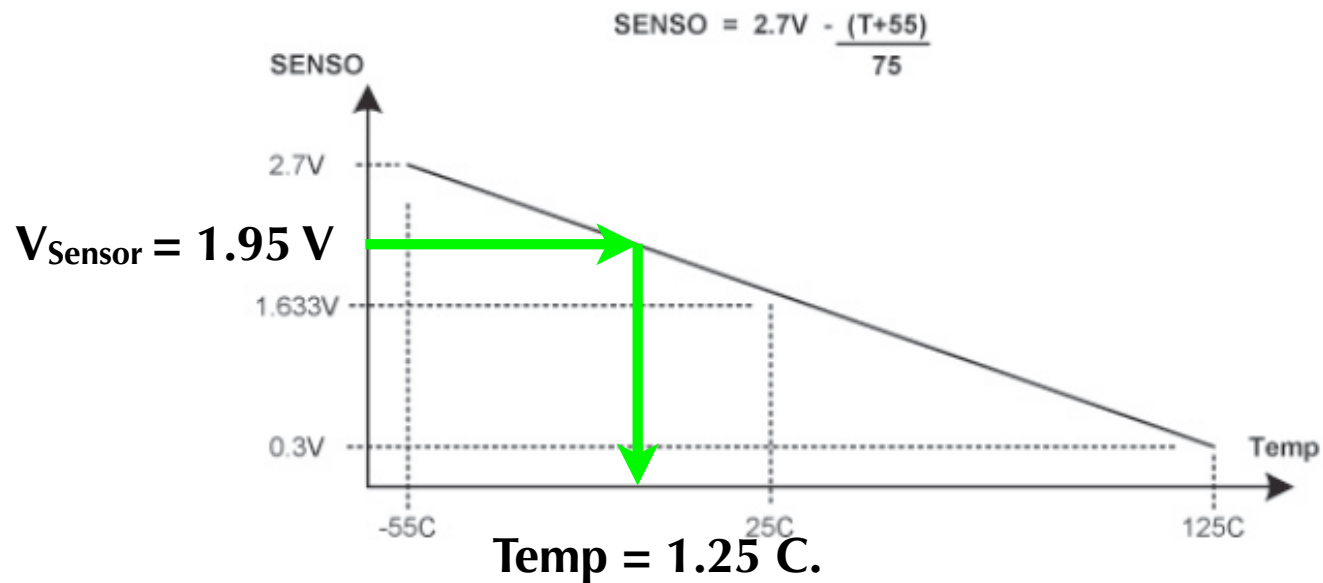

$$V_{\text{Sensor}} = 1.95 \text{ V}$$

$$\text{Temp} = - ((V_{\text{Sensor}} - 2.7 \text{ V}) * 75) - 55 = 1.25 \text{ C}$$

Non-Linear Sensors

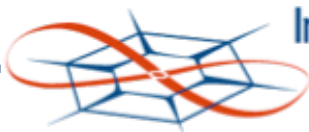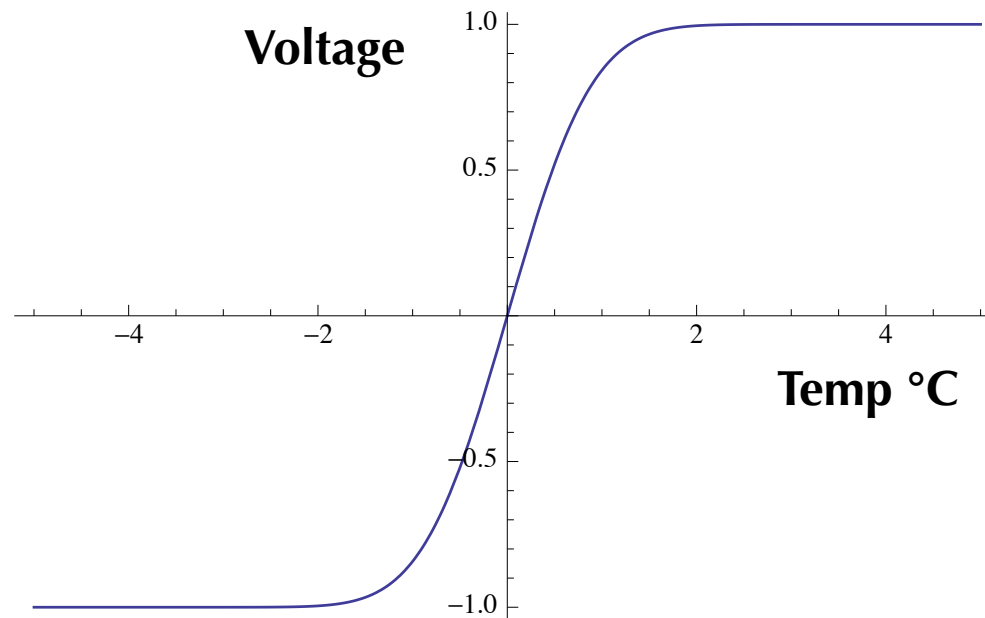

Information and
Telecommunication
Technology Center

KU THE UNIVERSITY OF
KANSAS


BMP 180 -- Reading Raw Values

read uncompensated temperature value
write 0x2E into reg 0xF4, wait 4.5ms
read reg 0xF6 (MSB), 0xF7 (LSB)
$UT = MSB \ll 8 + LSB$

read uncompensated pressure value
write $0x34 + (oss \ll 6)$ into reg 0xF4, wait
read reg 0xF6 (MSB), 0xF7 (LSB), 0xF8 (XLSB)
$UP = (MSB \ll 16 + LSB \ll 8 + XLSB) \gg (8 - oss)$

`bmp180_get_ut`
 UT = **27898** long
 oss = 0
 = *oversampling_setting*
 (*ultra low power mode*)
`bmp180_get_up` short (0 .. 3)
 UP = **23843** long

BMP 180 -- Calculate Temperature

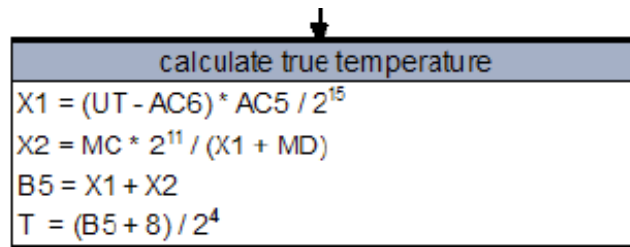

X1 = 4743
X2 = -2344
B5 = 2399
T = 150

bmp180_get_temperature
long
long
long
temp in 0.1°C long

BMP 180 -- Calculate Pressure

```

calculate true pressure
B6 = B5 - 4000
X1 = (B2 * (B6 * B6 / 212)) / 211
X2 = AC2 * B6 / 211
X3 = X1 + X2
B3 = (((AC1*4+X3) << oss) + 2) / 4
X1 = AC3 * B6 / 213
X2 = (B1 * (B6 * B6 / 212)) / 216
X3 = ((X1 + X2) + 2) / 22
B4 = AC4 * (unsigned long)(X3 + 32768) / 215
B7 = ((unsigned long)UP - B3) * (50000 >> oss)
if (B7 < 0x80000000) { p = (B7 * 2) / B4 }
    else { p = (B7 / B4) * 2 }
X1 = (p / 28) * (p / 28)
X1 = (X1 * 3038) / 216
X2 = (-7357 * p) / 216
p = p + (X1 + X2 + 3791) / 24
    
```

		BMP180_calpressure
B6 =	-1601	long
X1 =	1	long
X2 =	56	long
X3 =	57	long
B3 =	422	long
X1 =	2810	long
X2 =	59	long
X3 =	717	long
B4 =	33457	unsigned long
B7 =	1171050000	unsigned long
p =	70003	long
		long
X1 =	74529	long
X1 =	3454	long
X2 =	-7859	long
p =	69964	press. in Pa long

BMP 180 -- Altitude

$$\text{altitude} = 44330 * \left(1 - \left(\frac{p}{p_0} \right)^{\frac{1}{5.255}} \right)$$

Thus, a pressure change of $\Delta p = 1\text{hPa}$ corresponds to 8.43m at sea level.

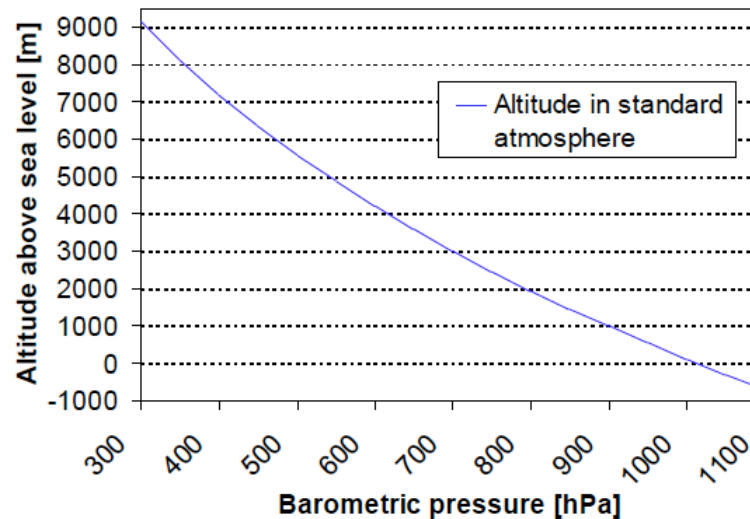


Figure 5: Transfer function: Altitude over sea level – Barometric pressure